

2 STAGE

COCKCROFT WALTON VOLTAGE MULTIPLIER


Submitted by:-

Amit Raj
(2023EEM1040)




Submitted to:-

Prof. C.C Reddy
(HOD, Electrical)

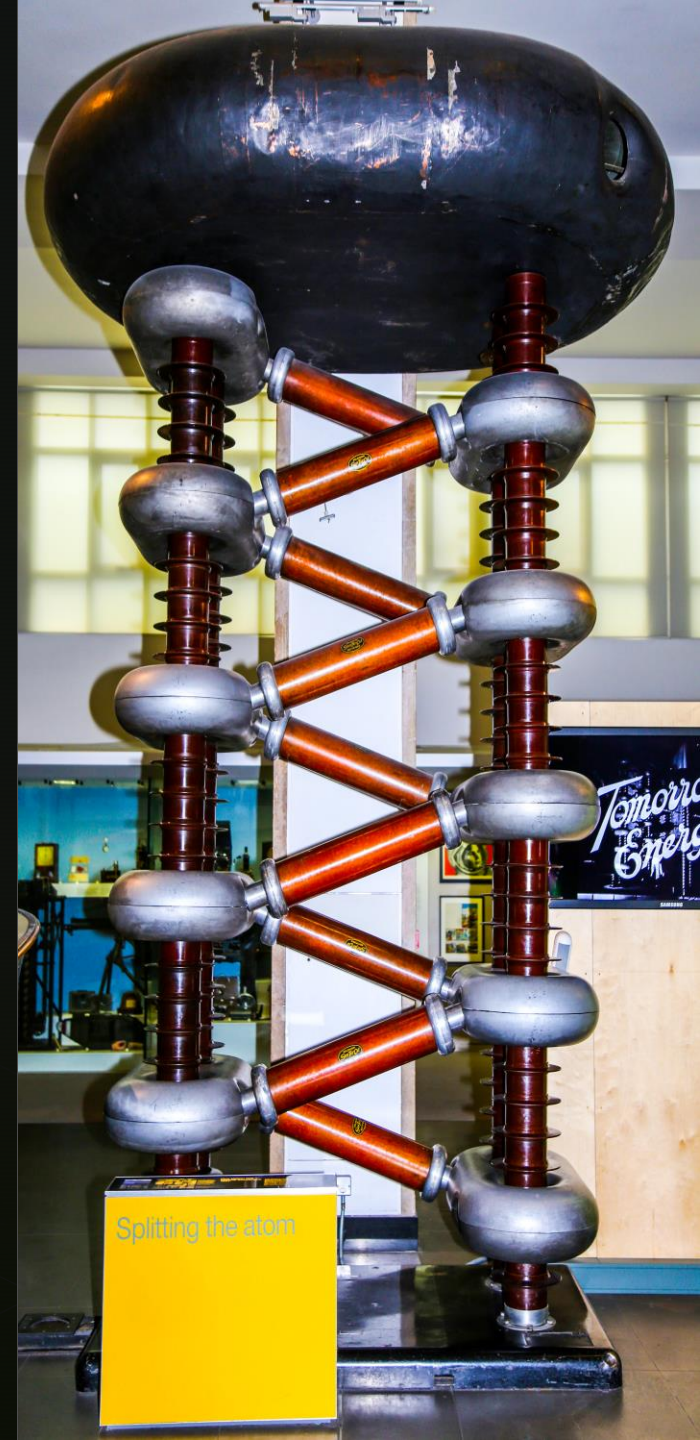


Theory

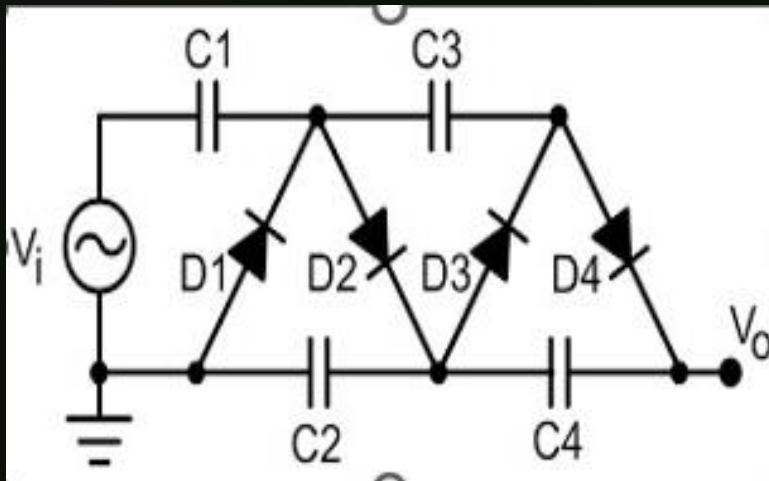
- About Cockcroft Walton Multiplier
- Working
- Reduction in Voltage




CIRCUIT DIAGRAM

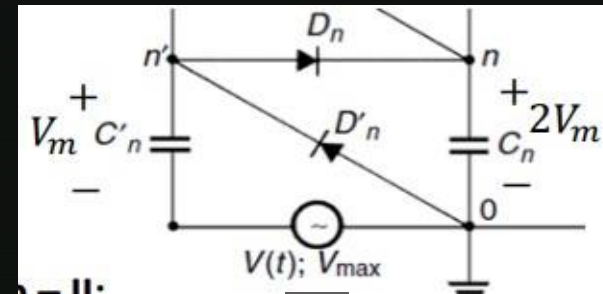

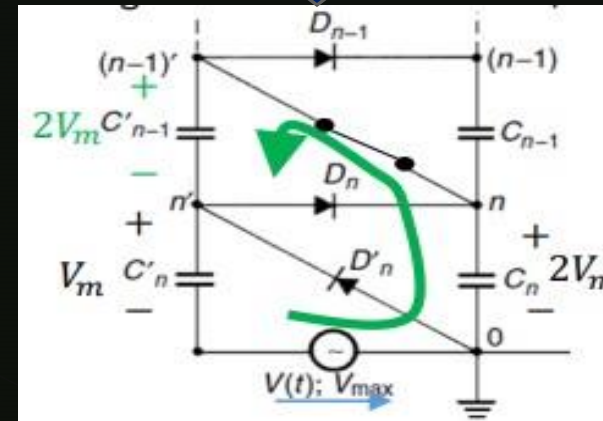Bottom stage charging is same as that of voltage doubler



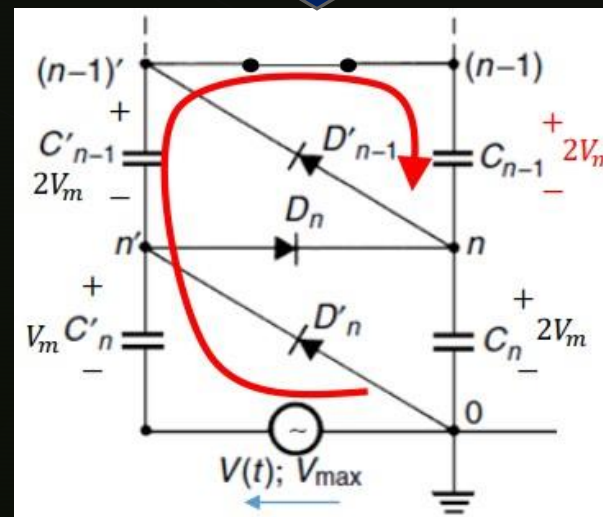Bottom stage diode will not activate, next stage diodes will activate



Positive half cycle

RATINGS AND CALCULATION

- CAPACITANCE(SMOOTHING COLUMN AND OSCILLATING COLUMN)
= 470uF , 100 volt
- TRANSFORMER RATINGS = 16 Volt , 1 Amp
- LOAD CAPACITANCE= C5= 22uf ,100 volt + C6= 2.2 uF 160Volt
- LOAD RESISTANCE = 26 kohm
- DIODE= If= 1 A , Vrrm= 1000 Volt

CALCULATIONS

Input Voltage =16 Volt


Let Ripple = 30% of No load Voltage = 2.75 Volt

I (current)= Ripple * 2 * f * C = 2.757 * 2 * 50 * 47 * 10⁻⁶ = 2. 16 mA

Reduction In Voltage = $\frac{I}{P_C} \left(\frac{n^3}{3} + \frac{n^2}{2} - \frac{n}{6} \right) = 6.434 \text{ V}$


Output Voltage = 2nVm - ΔVm = 90 . 5 – 6.434 = 84.066

RIPPLE FACTOR= ΔV/Vmean = 0.081

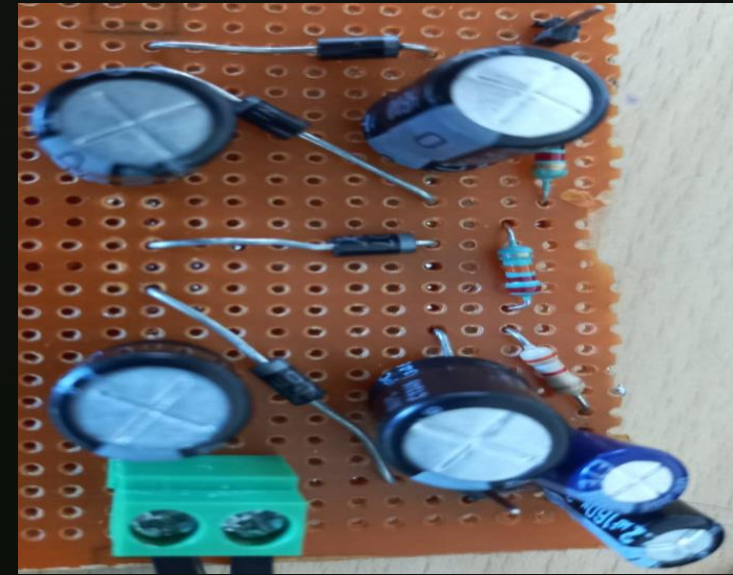


Hardware Model

SIMULATION

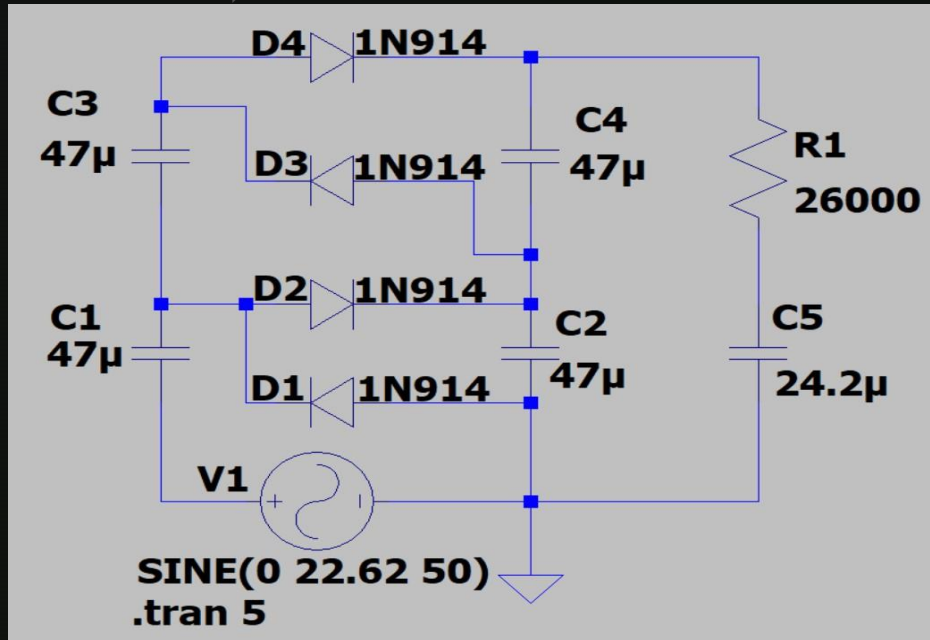


CIRCUIT DIAGRAM

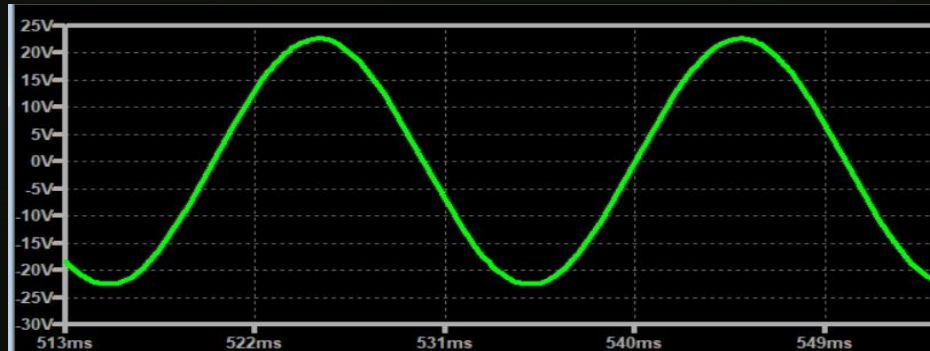


Input from transformer [$V_{rms} = 16V$
 $V_{peak} = 22.62$]


Results and Discussion

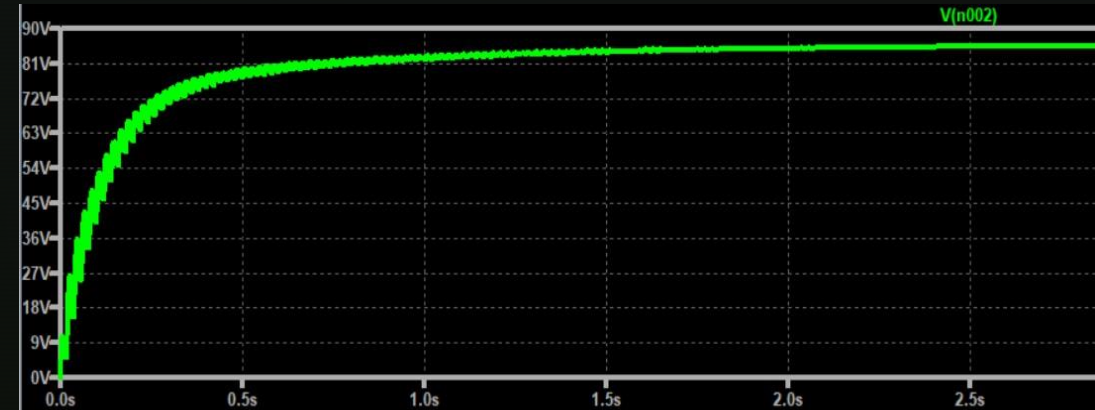

Output voltage = 85.83 volt

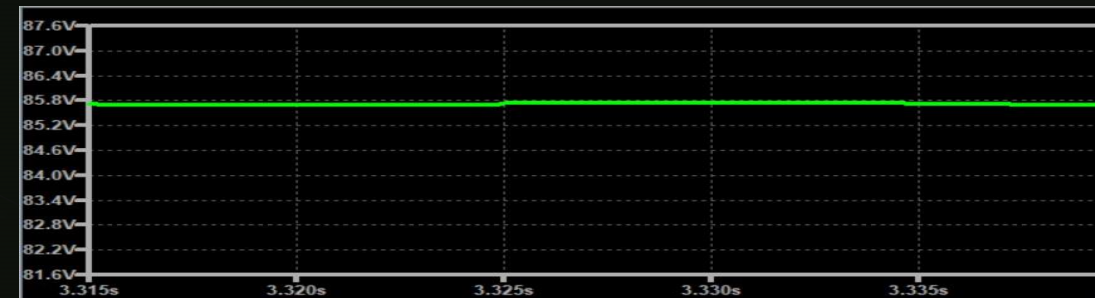


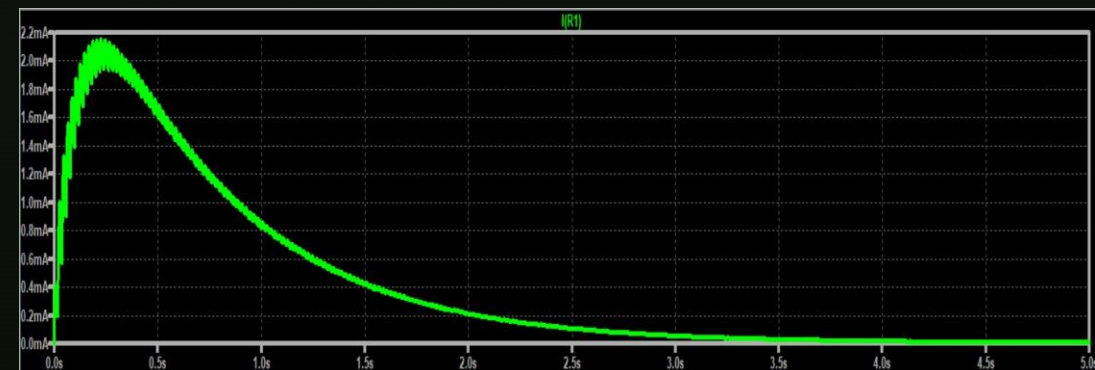Negligible ripple of 0.02 volt after 3 sec



Output current , $I_{max} = 2.16$ mA

HARDWARE RESULTS AND DISCUSSION

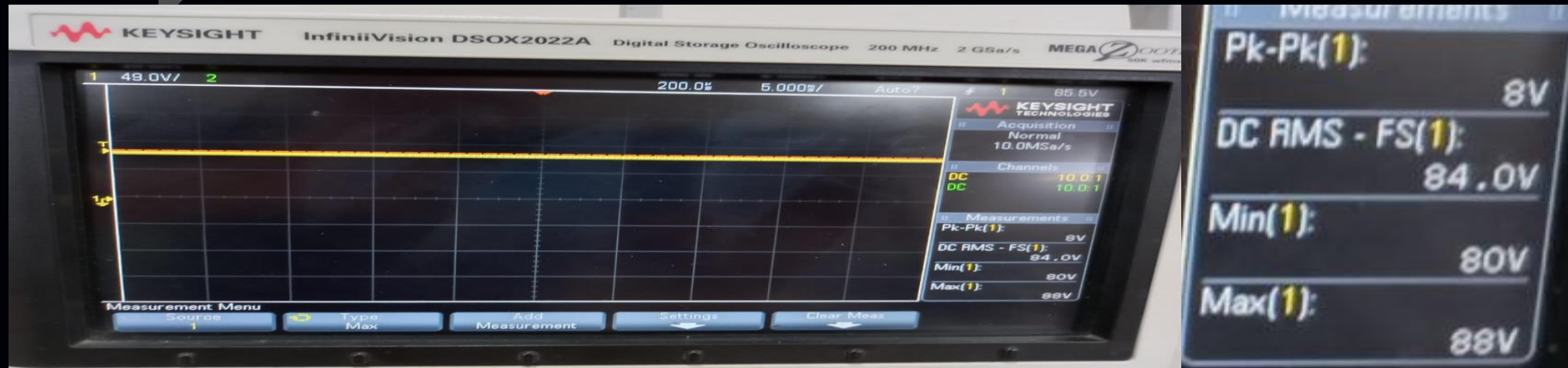

$V_{outRms} = 84 \text{ Volt}$ and Ripple is minimal

SL.no	Parameters	simulation	Hardware
1	Rms Output Voltage	85.83 volt	84.0Volt
2	Maximum Output current	2.16 mA	2.18 mA
3	Maximum Voltage Ripple	7 volt	8 volt
4	Ripple Factor	0.081	0.095
5	Reduced Voltage	4.6 volt	6.5 volt
6	Efficiency	95.3 %	93.34%